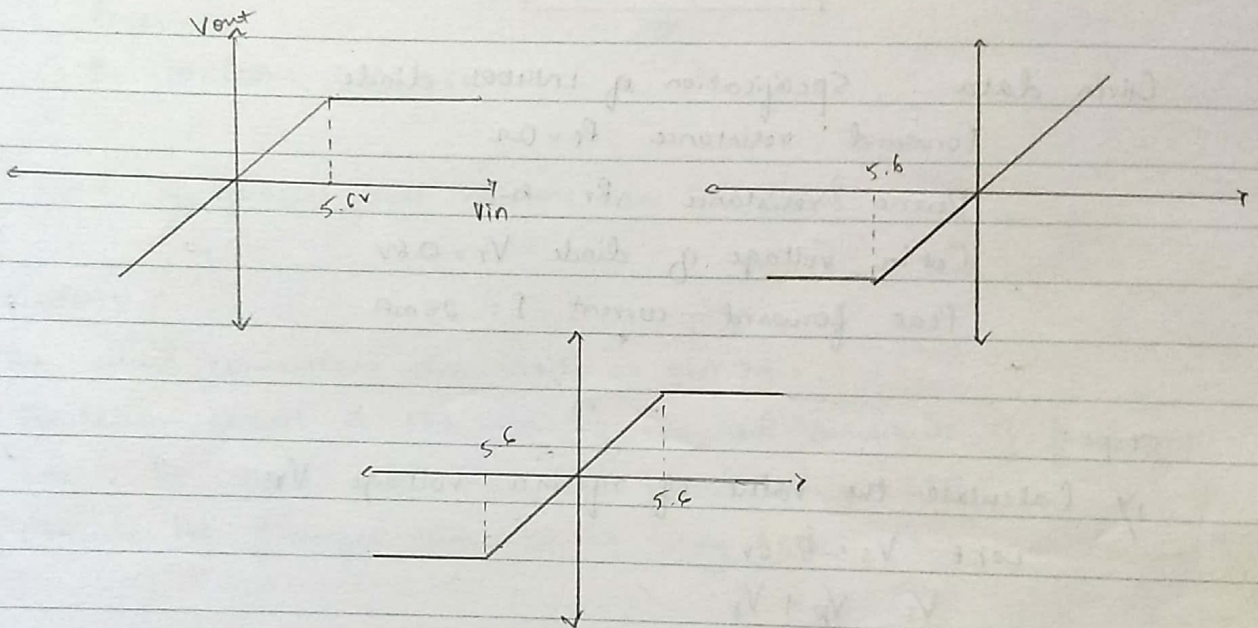


Experiment no: 1

Title: Design and testing of diode clipping circuits.

Aim: To design suitable diode clipping circuits for the transfer characteristics using 1N4001 diode with peak current $\leq 20\text{mA}$ and input signal will be $V_s = 8\sin(2\pi \times 10^3 t)$ volts.




List of components.

S.No	Components	Specification	Quantity
1	Diodes	1N4001	02
2	Resistor	$1\text{k}\Omega$	01
3	AFO	3MHz , 20V_{pp}	01
4	CRO	20MHz , 70V_{pp}	01
5	DC power supply	0.3V , 2A	01
6	BNC's	--	03

Formula Required / Design:

Positive clipper:

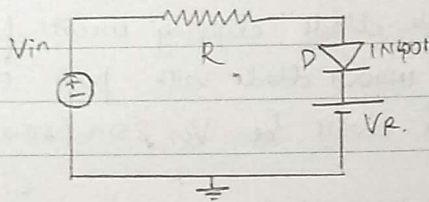The transfer characteristics in first figure is of positive clipper and circuit is



Given data: Specification of 1N4001 diode

Forward resistance $R_f = 0.2$

Reverse resistance $R_r = \infty$

Cut in voltage of diode $V_r = 0.6V$

Peak forward current $I = 25mA$

Steps:

1) Calculate the value of reference voltage V_R

$$\text{wkt } V_s = 5.6V$$

$$V_s = V_R + V_r$$

$$V_R = V_s - V_r = 5.6 - 0.6 = 5V$$

2) Compute value of R required.

by KVL we have

$$V_s(t) = I_s(t)R + V_r + V_R$$

under maximum conditions

$$V_m = I_m R + V_r + V_R$$

$$8 = 25m \times R + 0.6 + 5$$

$$R = \frac{8 - 5.6}{2.5} k\Omega = 0.96 k\Omega$$

Standard value of resistor near to 0.96 is $1k\Omega$

3/ To decide the wattage of resistor, first we have to calculate power.

$$P_{D(R)} = \frac{I_m^2 R}{2} = \frac{(2.5 \times 10^{-3})^2 \times 10^3}{2}$$

$$P_{D(R)} = 3.125 \text{ mW}$$

4/ Power rating of resistor should be 10 times larger than $P_{D(R)}$


$$P = 10 \times P_{D(R)} = 0.03125 \text{ W}$$

Hence a quarter watt resistor can be used.


Procedure:

- The circuit connections are made as shown.
- For each circuit a sine wave of required amplitude & frequency has to be given and output is traced using CRO.
- Observe the transfer characteristics using CRO.

Circuit Diagram

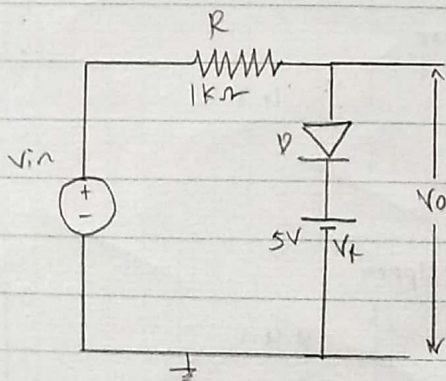

Positive clipper

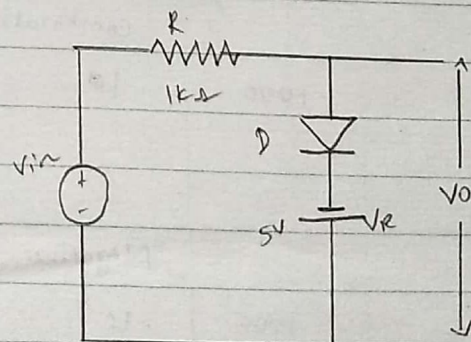

Negative clipper.

Combination Clipper

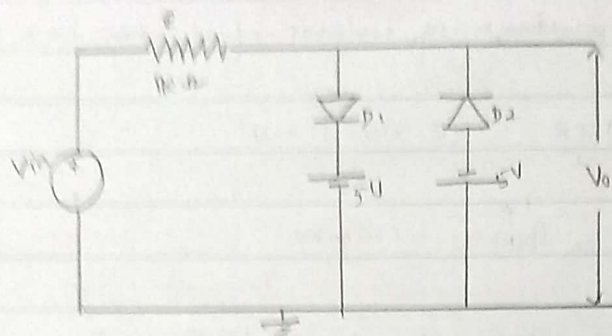


Table of observation

Sr No	$V_{ref} = V_R$ in V	Frequency in Hz	V_{in-p-p} in V	V_{op-p} in V	Clipped portion $V_{in-p-p} - V_{op-p}$ in V
Positive unbiased clipper					
1	0	1000	16	8.6	7.4
Negative unbiased clipper.					
1	0	1000	16	8.6	7.4
Positive biased clipper					
1	5	1000	16	13.6	2.4
2	-5	1000	16	3.6	12.4
Combinational clipper					
1	5	1000	16	11.2	4.8
Negative biased clipper					
1	5	1000	16	13.6	2.4
2	-5	1000	16	3.6	12.4

EXPERIMENT NO.:



SCALE:

X - axis:

DATE:

Y - axis:

combinational digpen.

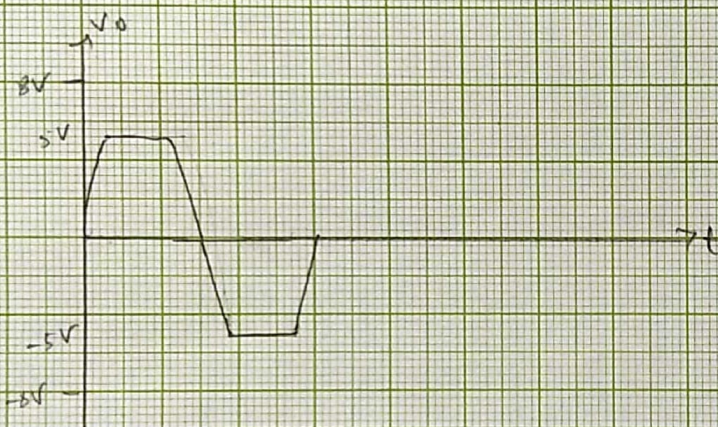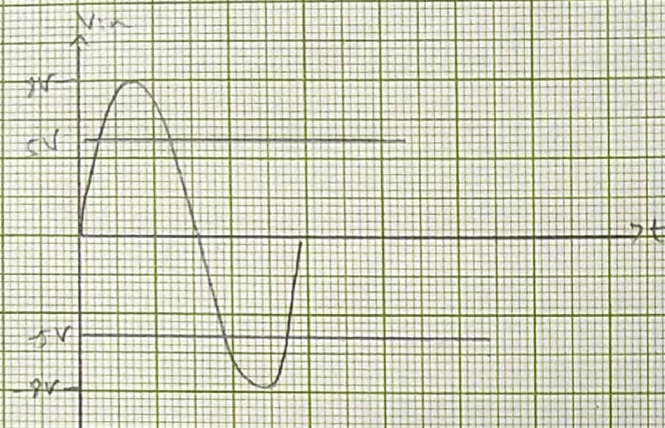

EXPERIMENT NO. :

DATE :

SCALE :

X - axis :



Y - axis :

Positive Clipper

Negative Clipper





V_{in} with +ve dc ref

V_{in} with -ve dc ref

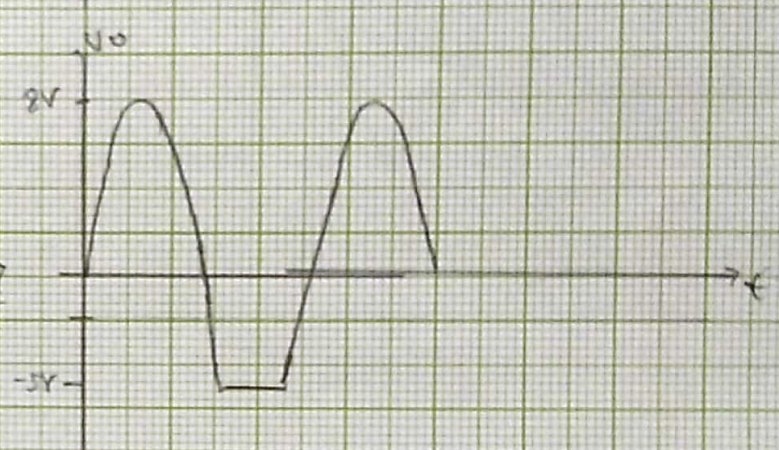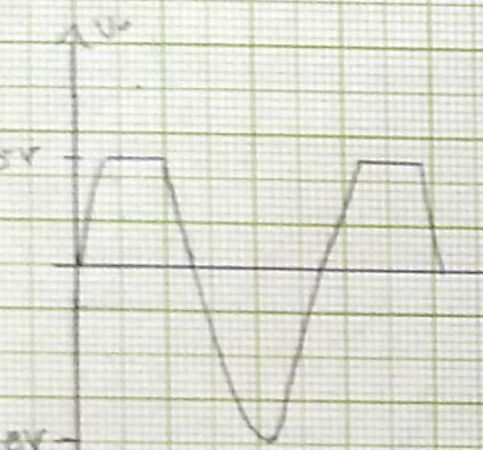


V_{in} with -ve dc ref

V_{in} with +ve dc ref

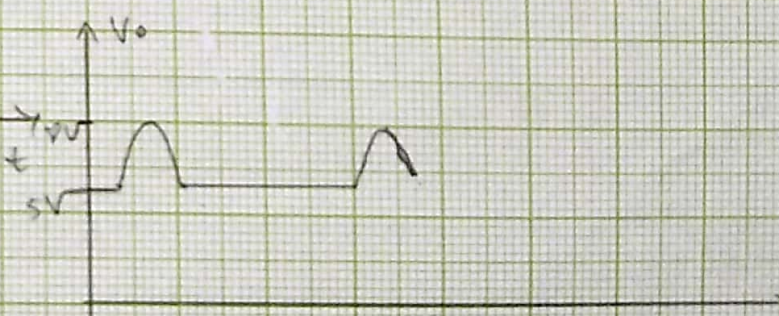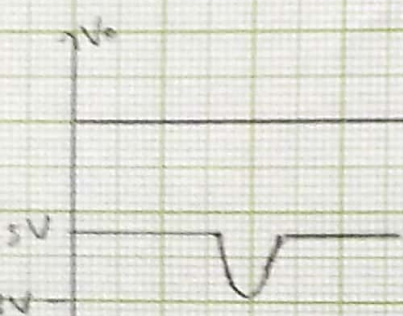
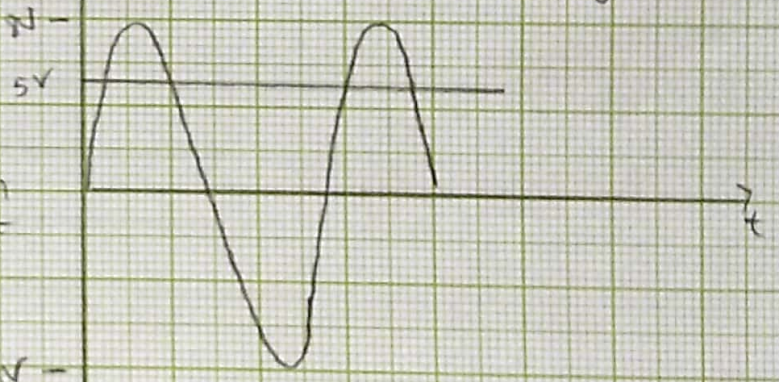
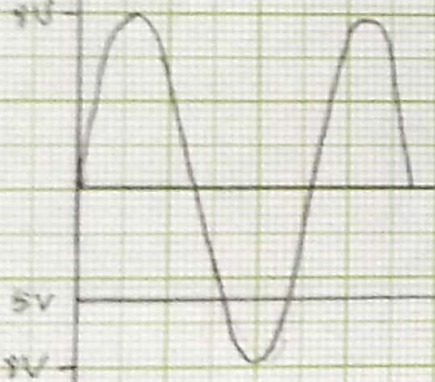


Nature of graph:



Positive clipper

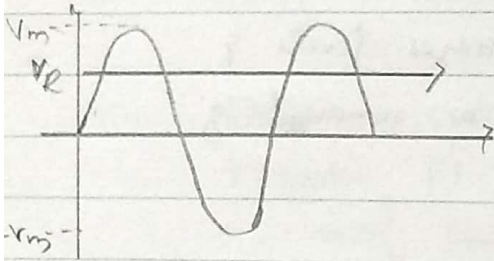

Negative clipper

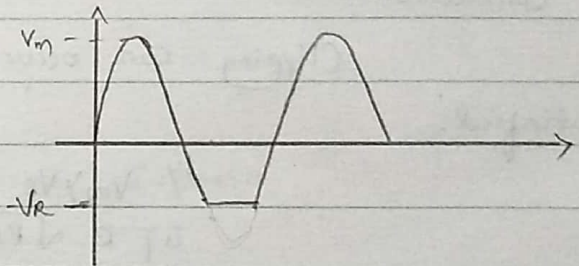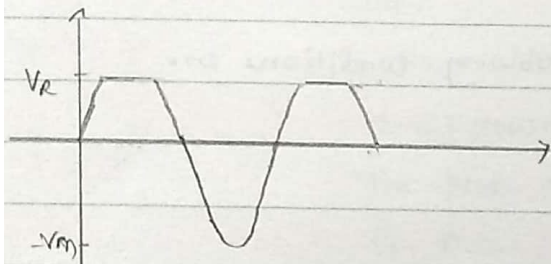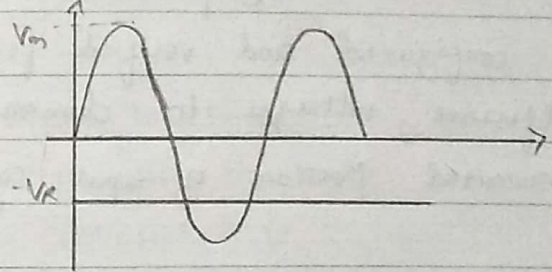

Combinational clipper

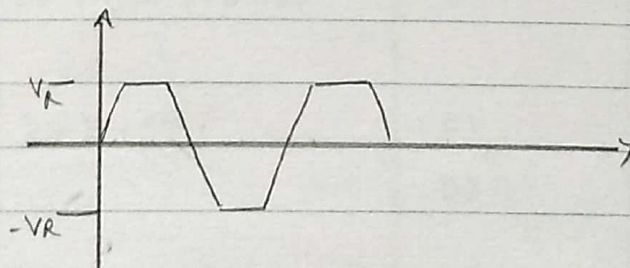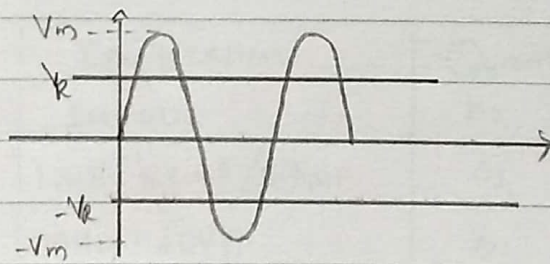

Conclusion of experiment

Result & Discussion

Experimental setup for clipping circuit using diode is configured and verified for different input voltages levels & reference voltages to demonstrate the clipping or removal of unwanted portion of input signal.

Conclusion:

Clipping can occur only when following conditions are satisfied.

$$\begin{aligned} \text{i) } V_m > V_R \\ \text{ii) } R < \sqrt{R_1 R_2} \end{aligned}$$

Experiment no :

Title : Design and testing of diode clamping circuits.

Aim : Design a suitable circuit using diode to clamp
i) negative ii) Positive extremity of a periodic signal to
zero volts. For input $v_s(t) = 5 \sin(2\pi \times 10^3 t)$ V.

Given

diode 1N4001

Breakdown voltage = 50V

The peak representative current $\leq 100\text{mA}$

$R_f = 0\Omega$


$R_r = \infty$

$V_r = 0.6\text{V}$


List of components :

Sl No	Components	Specification	Quantity	Cost per item
1	Diodes	1N4001	02	2
2	Capacitors	1 μF / 0.1 μF / 4.7 μF	01	5
3	AFO	1MHz, 20Vpp	01	10,000
4	CRO	20 MHz, 80Vpp	01	25,000
5	Power supply	30V, 2A	01	4,000
6	BNC's		03	150

Design:

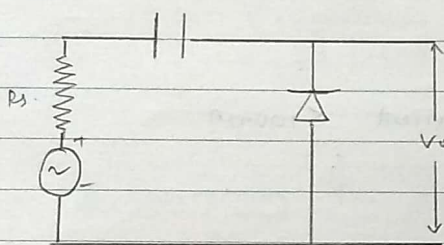Maximum current $I_{max} = 1A$ Maximum peak current $I_{peak} = 20A$ Breakdown voltage $-50V$ Large signal parameter $V_r = 0.6V$ $R_f = 0.2$ $R_r = \infty$ Input signal $V_s = 5 \sin(2\pi \times 10^3 t)$ volts.Output voltage $V_o = 2V_m$.

Positive clamper circuit

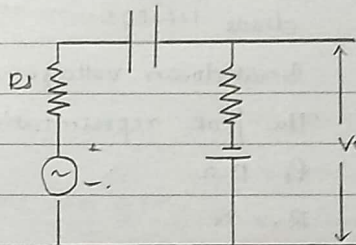

Equivalent ckt when diode is forward biased.

Design steps:

1) Compute the value of capacitor C

Replace diode with equivalent circuit when diode is forward biased, then applying theorems wkt

$$Z = \sqrt{R^2 + X_c^2}$$

$$Z = \sqrt{(R_s + R_f)^2 + \left(\frac{1}{\omega C}\right)^2}$$

2) Applying KVL to ckt

$$V_s(t) = I_s(t) Z - V_r$$

Since $V_r \leq V_s(t)$

$$V_s(t) = I_s(t) \sqrt{(R_s + R_f)^2 + \left(\frac{1}{\omega C}\right)^2}$$

under max condition

$$V_m = I_m \sqrt{(R_L + R_S)^2 + X_C^2}$$

$$I_m = \frac{V_m}{\sqrt{(R_L + R_S)^2 + X_C^2}} \leq 100 \text{ mA}$$

47 Consider forward resistance of diode R_f & internal resistance of generator R_s to be very small & neglect them.

$$I_m = \frac{V_m}{\sqrt{(1/\omega C)^2}} \quad V_m \omega \leq 100 \text{ mA}$$

57 Rearranging the equation we get


$$C = \frac{I_m}{V_m \omega} = \frac{100}{5 \times 2\pi \times 10^3} = 3.18 \mu\text{F}$$

67 The nearest standard capacitor value is $4.7 \mu\text{F}$


77 In order to find the PIV rating of the diode consider the case when diode is not conducting i.e. during the positive half cycle hence

PIV = $2V_m = 10\text{V}$, it should be less than breakdown voltage.

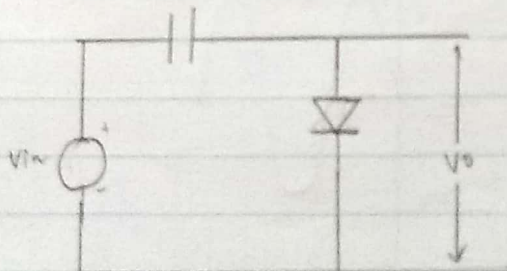
87 Hence Capacitor voltage rating may be 10V .




i) Positive biased clamper

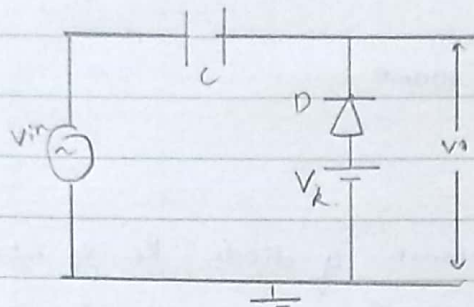

ii) Negative clamper circuit.

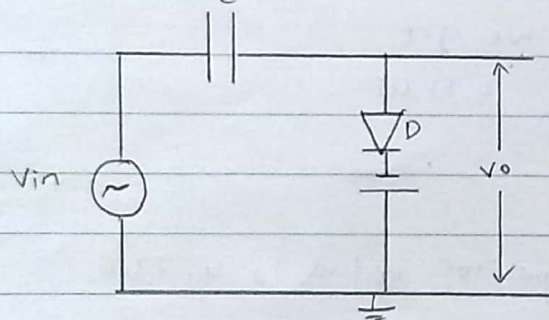

Nature of graph

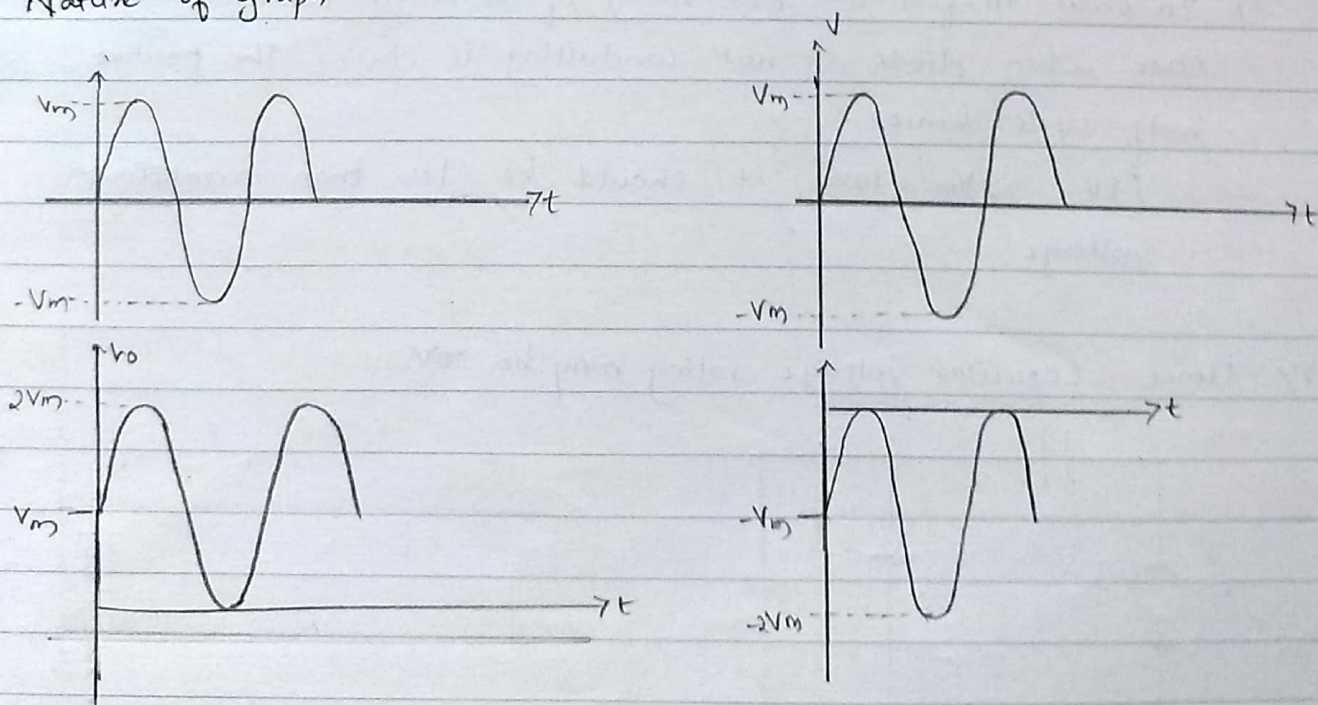


EXPERIMENT NO.:

DATE:

SCALE:

X - axis :

Y - axis :

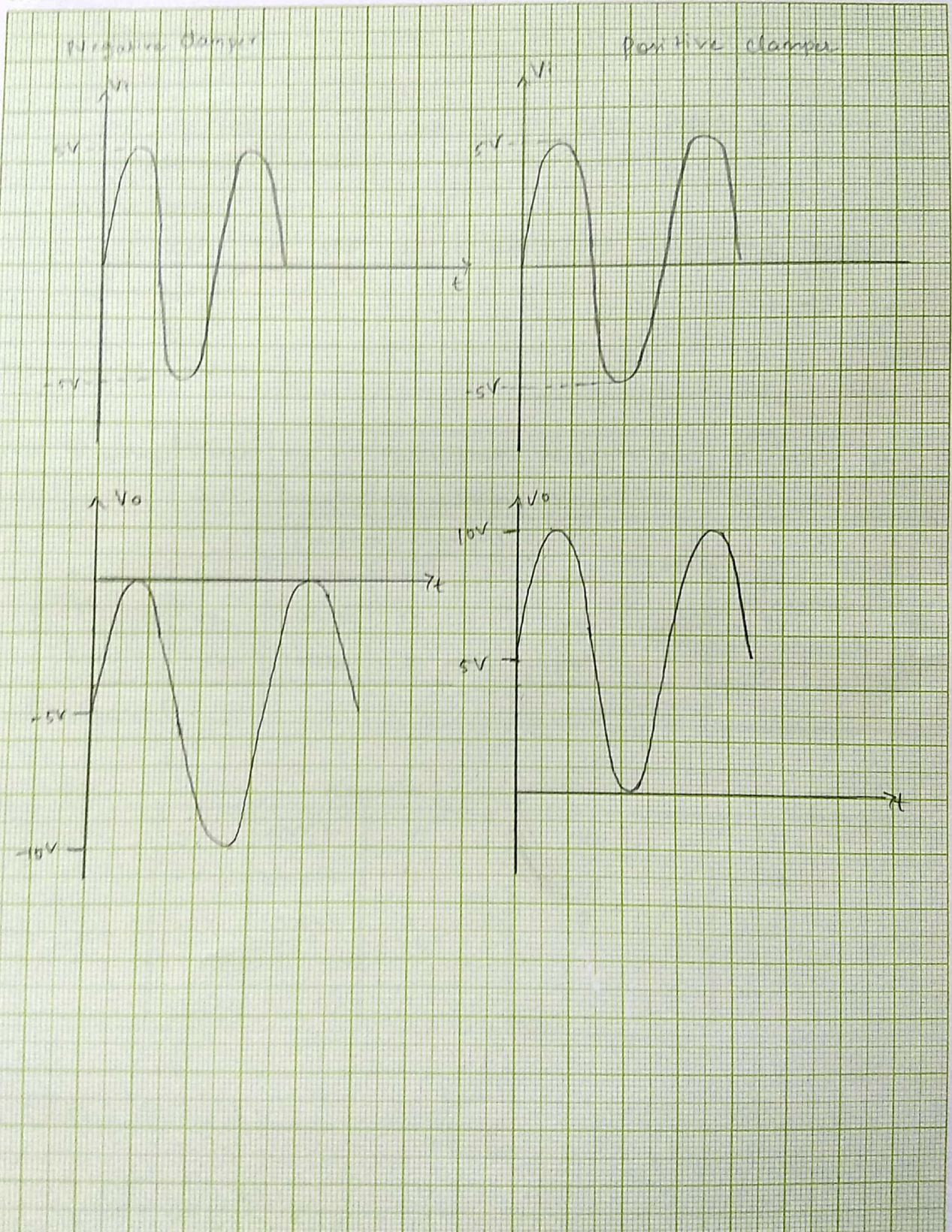

Procedure:

1) The circuit connections are made as shown in the circuit diagram.

2) For each circuit give a sine wave input of desired amplitude and frequency as input is shown and note down output wave form as seen in CRO.

3) Keep the CRO on DC mode to observe the output wave form.

Table of observation:

S.No	i/p voltage	V _{ref} in Volts	i/p frequency	Positive peak o/p voltage	Negative peak o/p voltage	Average o/p Voltage
Positive clamper						
1	5V	0V	1000Hz	10	0V	5V
2	5V	2V	1000Hz	12	2V	7V
3	5V	-2V	1000Hz	8	-2V	3V
Negative clamper						
1	5V	0V	1000Hz	0	-10	-5
2	5V	2V	1000Hz	-2	-12	-7
3	5V	-2V	1000Hz	2	-8	-3

Experiment no.:

Title: Realization of BJT as a switch.

Aim: Design a switch using BJT with following specifications

i) $\beta = 50 - 150$


ii) Overdrive factor = 10

iii) $V_{CC} = 5V$ iv) $R_C = 1K\Omega$ v) $V_{CEsat} = 0.2V$

List of components.

Sl No	Components	Specification	Quantity
1	BJT	2N2222A	1
2	Variable power supply	0.3V, 2A	2
3	Voltmeter	0-10V	
4	Resistor	$R_C = 1K\Omega, 0.25W$ $R_B = 2.2K\Omega, 0.25W$ $R_C = 1K\Omega, 0.25W$	
5	Wires		Assorted.

Design:

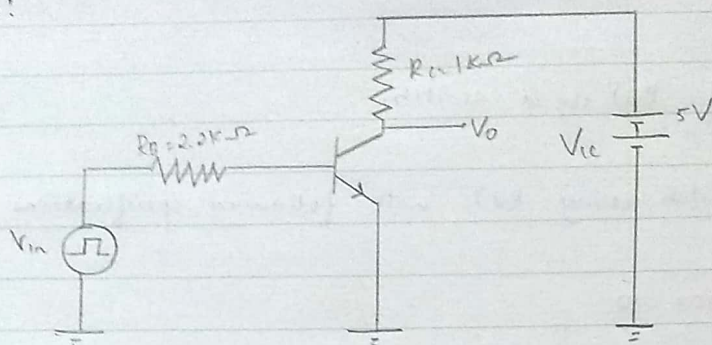

Design steps:

- 1) When the transistor is in saturation the collector voltage will be

$$V_c = V_{c\text{sat}} = 0.2V$$

- 2) The collector current is given by

$$I_{c\text{sat}} = \frac{(V_{cc} - V_{c\text{sat}})}{R_c}$$

$$= \frac{5 - 0.2}{1k} = 4.8 \text{ mA}$$

- 3) To saturate the BJT with the lowest β , we need to provide a base current of atleast

$$I_{B\text{EOS}} = I_{c\text{EOS}} / \beta = \frac{4.8 \text{ mA}}{30} = 0.16 \text{ mA}$$

- 4) For an overdrive factor of 10, the current should be atleast

$$I_B = 10 \times I_{B\text{EOS}} = 1.6 \text{ mA}$$

- 5) Required R_B is

$$R_B = \frac{(V_B - V_{BE})}{I_B} = \frac{5 - 0.7}{1.6} = 2.6 k\Omega$$


EXPERIMENT NO.:

SCALE:

X - axis:

DATE:

Y - axis:

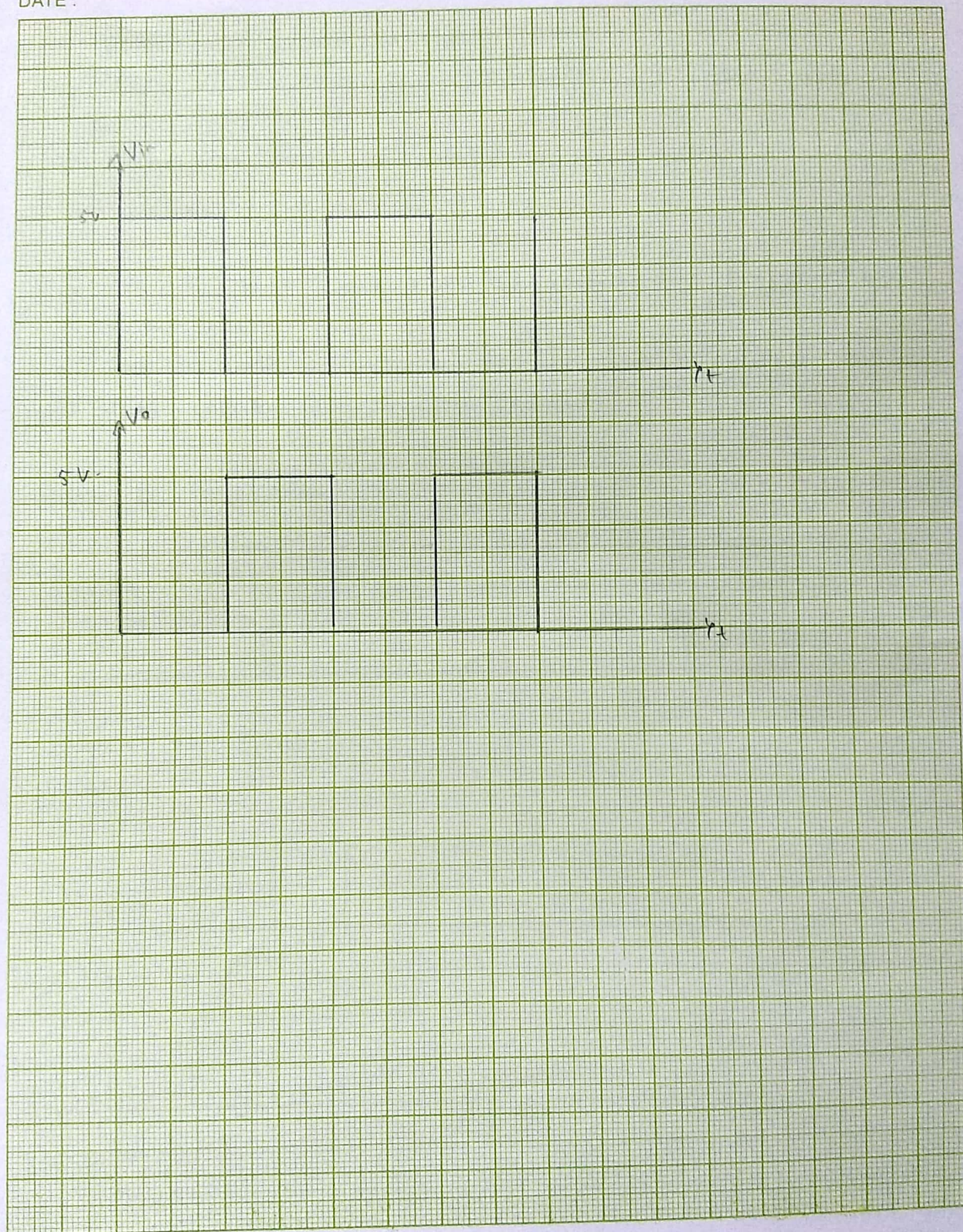

Procedure :


- i) Connect the circuit as shown .
- ii) Apply a 5V , 2KHz pulse signal with 50% duty cycle as input.
- iii) Observe the output at collector terminal voltage.

OR

- i) Set V_B to 0V and note the corresponding output voltage across collector and emitter terminal .
- ii) And similarly set V_B to 5V and note the output voltage across collector and emitter terminal.

Table of observation .

V_{in} in Volts	V_o in volts	BJT condition.
0V	5V	Cut-off
5V	0V	Saturation.

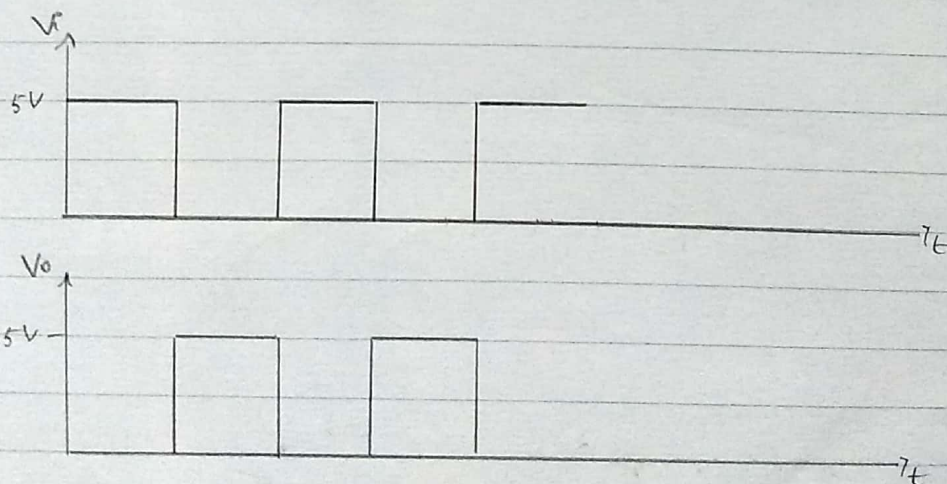Nature of Graph:

Result and Discussion :

Experimental setup for BJT as switch in CE configuration is done and tested for different input signals conditions to identify different regions of operation.

∴ Cut off and Saturation region.

To summarise BJT as a switch, input and output voltage observed are

- with $V_{BB} = 0V$, transistor is in cut-off region & hence output voltage $V_o = V_{CE}$.
- with $V_{BB} = 5V$, $V_{BE} = 0.6V$ transistor is operated in saturation region and hence output voltage $V_o = V_{CEsat} = 0.2V$.

Conclusion:

BJT a three terminal device working as voltage controlled current source can be used as a switch operating in two condition is ON & OFF. Finding major applications in realizing digital gates.